


SIMULATIONS

THEORETICAL DESIGN


SAMPLE VALUES

Component	Value
Fs	100kHz
T	$1 / 100k = 10\mu s$
Vin	12V
Vout	24V
Duty cycle	$12 / 24 = 0.5$
L1	100uH
Cout	100uF
Rload	100Ω

SIMULATION CIRCUIT

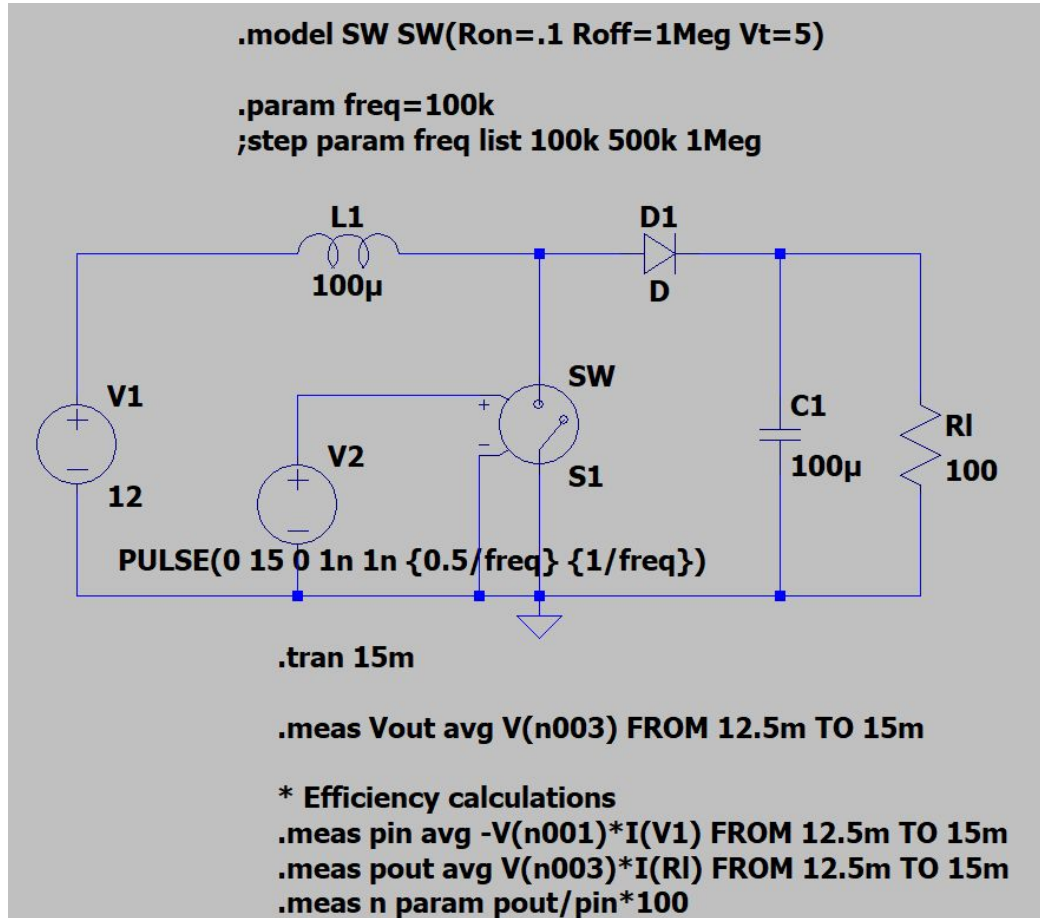


OUTPUT VOLTAGE PLOT

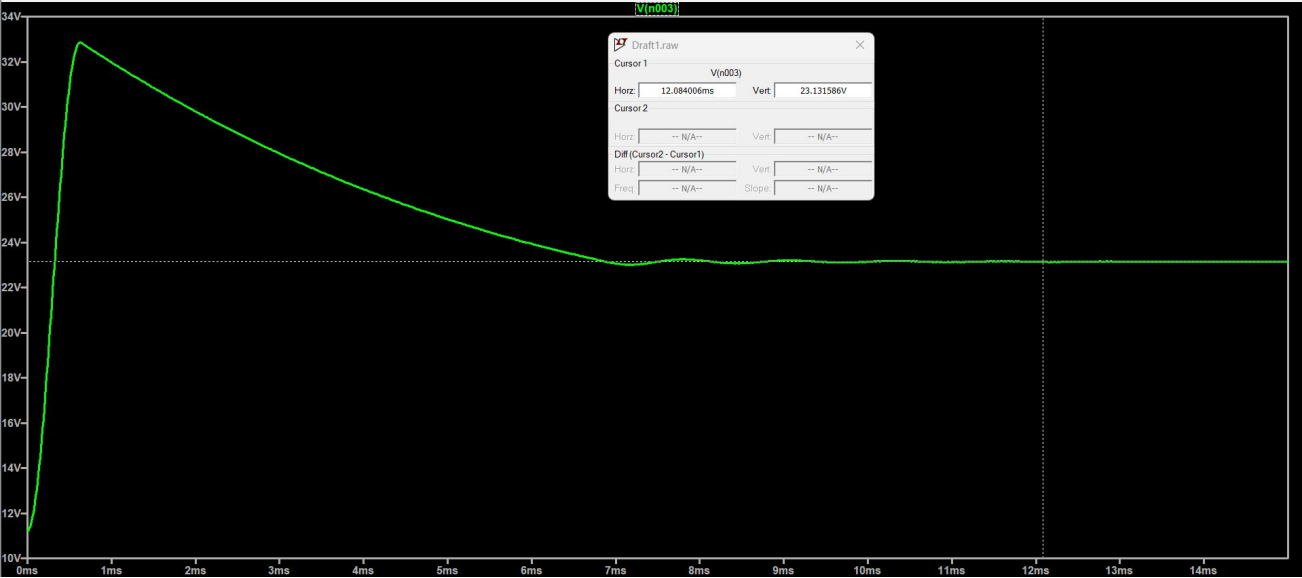

Parameter	Value
Vout	23.15V
Pin	5.56W
Pout	5.36W
n	96.38%


VARYING FREQUENCY: OUTPUT VOLTAGE

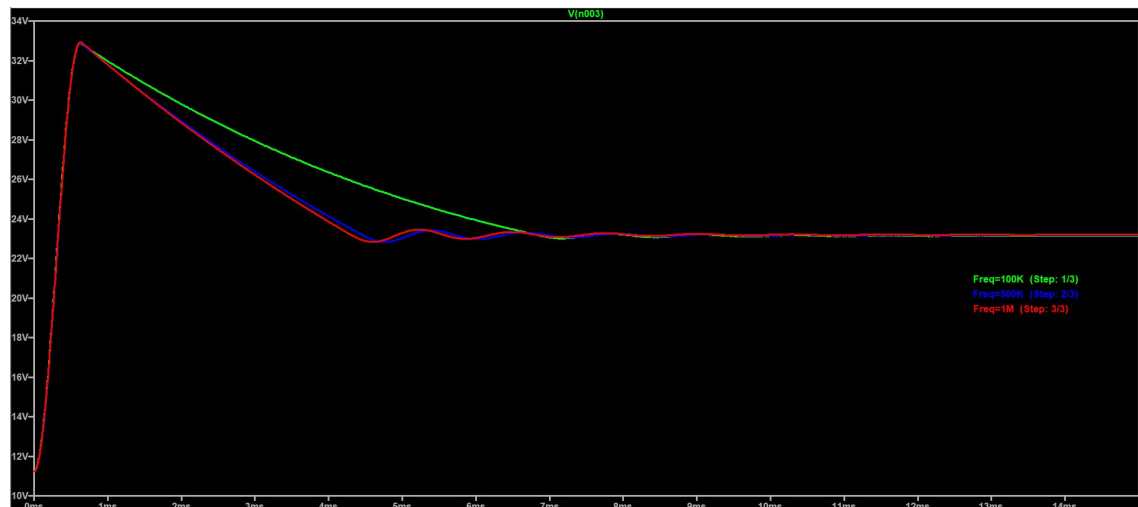

Measurement: vout				
step	AVG (V(n003))	FROM	TO	
1	23.145550036	0.0125	0.015	
2	23.1660674871	0.0125	0.015	
3	23.1928418999	0.0125	0.015	
Measurement: pin				
step	AVG (-V(n001) * I (V1))	FROM	TO	
1	5.55881920216	0.0125	0.015	
2	5.57092760152	0.0125	0.015	
3	5.57869524817	0.0125	0.015	
Measurement: pout				
step	AVG (V(n003) * I (R1))	FROM	TO	
1	5.35716519769	0.0125	0.015	
2	5.36666702304	0.0125	0.015	
3	5.37907934047	0.0125	0.015	
Measurement: n				
step	pout/pin*100			
1	96.3723590003			
2	96.3334548015			
3	96.42181731			

Output voltage trend	Higher frequency ensures inductor operates in CCM with current high for most of cycle, leading to better energy transfer and slight overshoot.
Transient time trend	The output capacitor C1 is charged more frequently per second, reducing the output ripple and significantly shortening the time required to reach a stable, final Vout.
Efficiency trend	Do not change since we are using ideal switch. If Mosfet is used, higher frequencies will lead to higher switching losses reducing efficiency.

VARYING FREQUENCY: INDUCTOR CURRENT


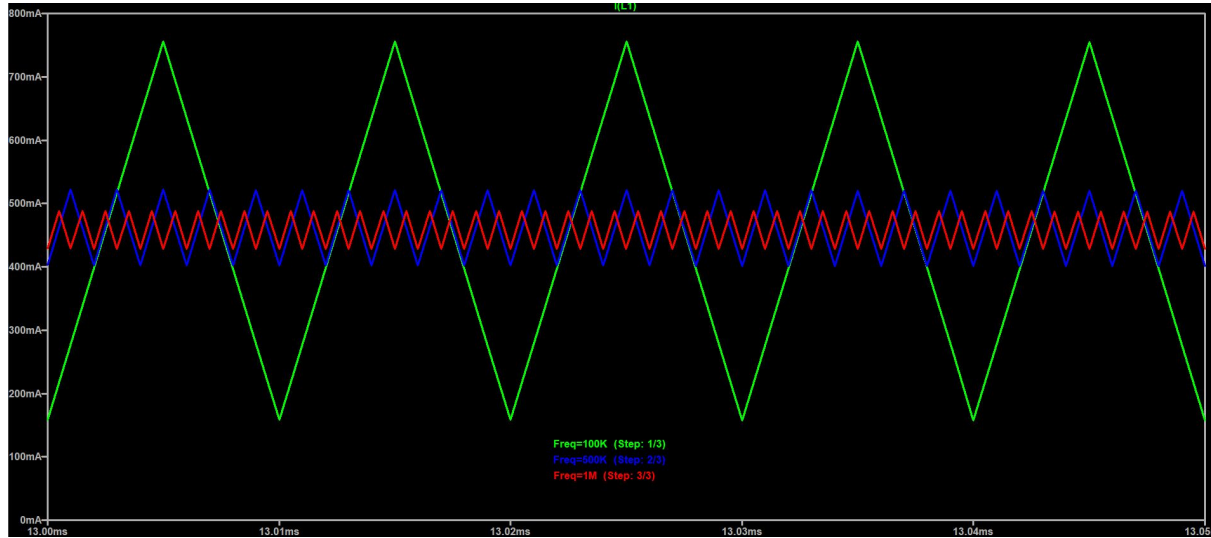


1. $V_{in}/L = di_L / dt$
Since V_{in} and L are constant slope is linear.
2. The rise and fall time are identical due to 50% duty cycle.

Since slope is linear we can use change instead of gradients:
$$\Delta I_L = V_{in} * T * D / L = (V_{in} * D) / (f_s * L)$$


Ripple	From formula we can see increasing frequency reduces ripple
Operation	All three frequencies are high enough to ensure CCM.
DC offset	In case of MOSFET we would expect current to have negative dc offset due to switching losses.

VARYING INDUCTOR: OUTPUT VOLTAGE

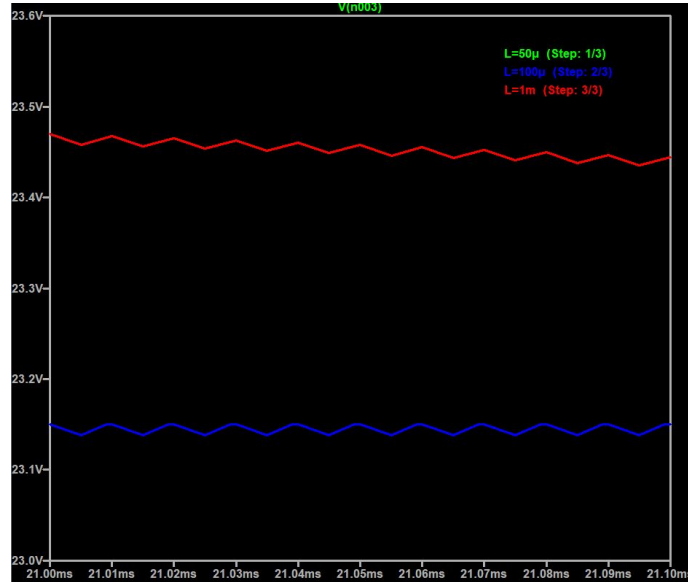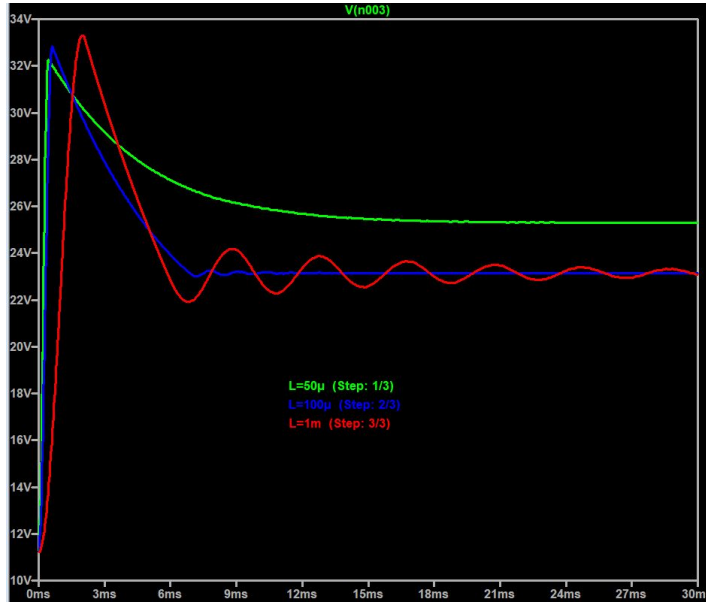

Transient time	V_{out} takes longer to settle, due to time constant being L / R
Ripple	Seems similar, theoretically have inverse relation.

VARYING INDUCTOR: INDUCTOR CURRENT


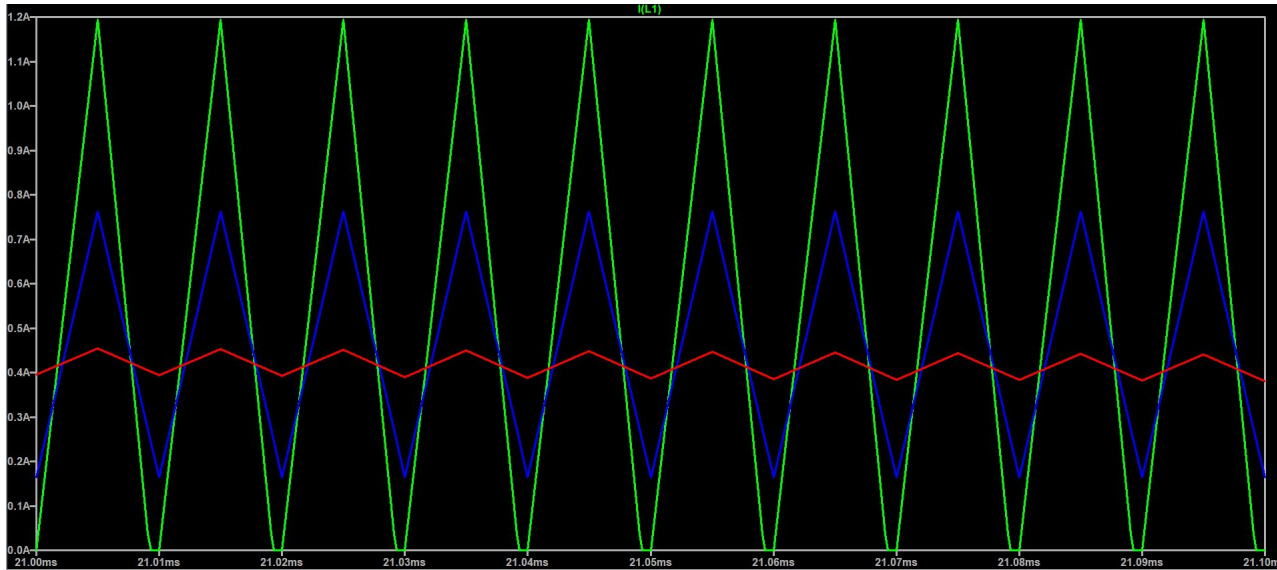


1. $V_{in}/L = diL / dt$
Since V_{in} and L are constant slope is linear.
2. The rise and fall time are identical due to 50% duty cycle.

Since slope is linear we can use change instead of gradients:
$$\Delta IL = V_{in} * T * D / L = (V_{in} * D) / (f_s * L)$$

Ripple	From formula we can see increasing inductance reduces ripple
Operation	For 50uH the converter operates in DCM and inductor current reaches 0.



VARYING CAPACITOR: OUTPUT VOLTAGE

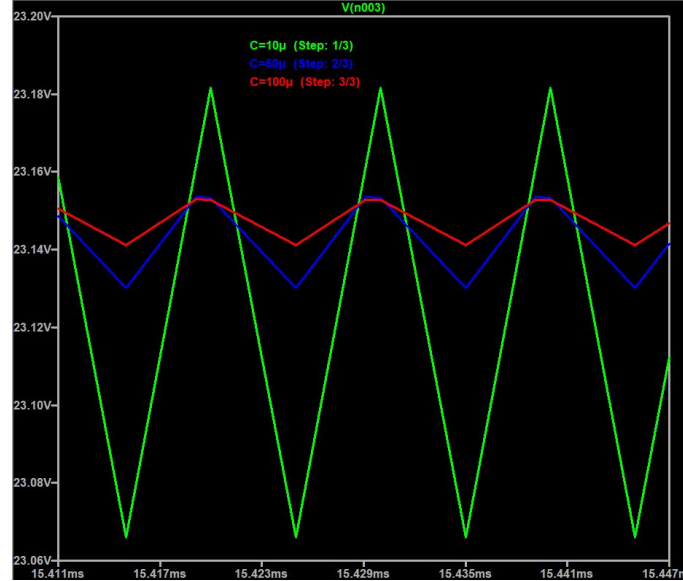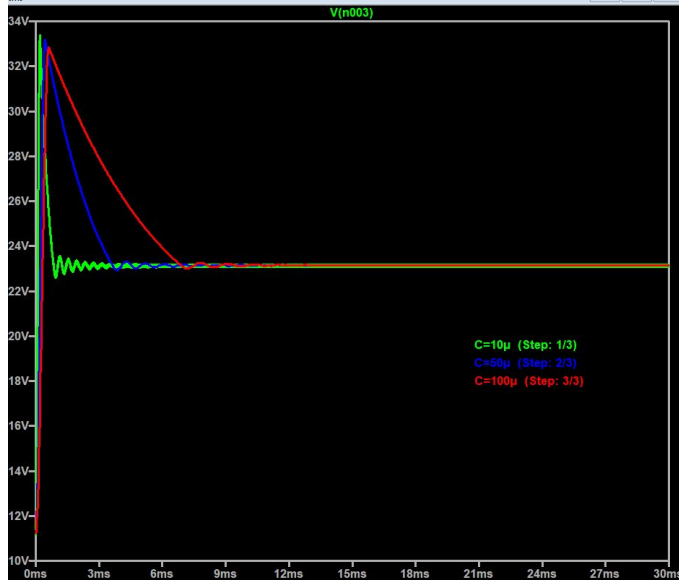

$$\Delta V_{out} = [I_{out_max} * D_{max}] / [f_s * C]$$

Transient time	Vout takes longer to settle (time constant = RC)
Ripple	Larger capacitor reduces ripple

VARYING RESISTOR: OUTPUT VOLTAGE

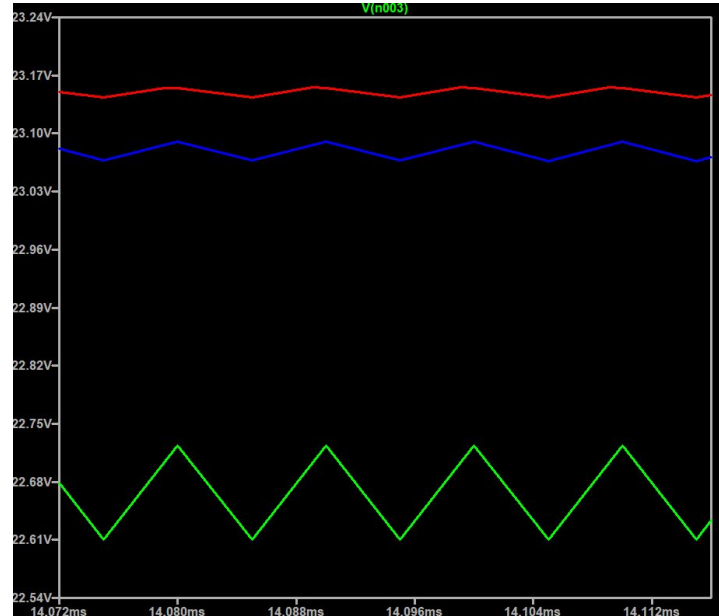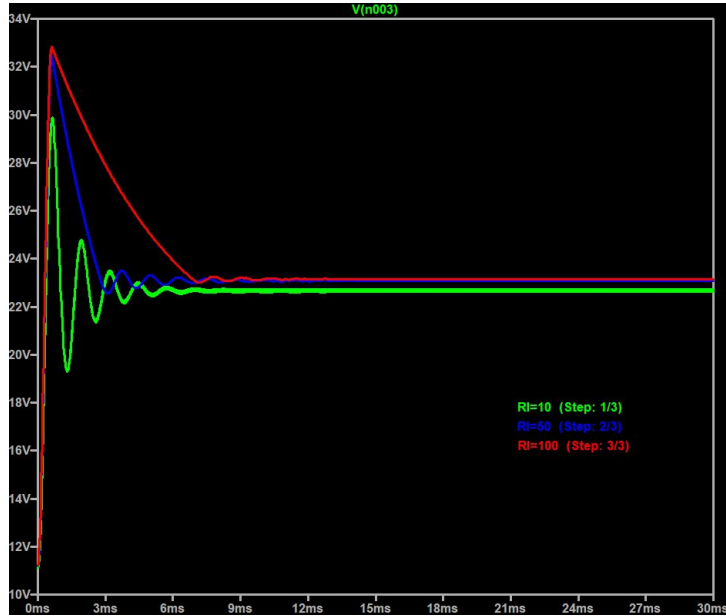

$$\Delta V_{out} = [I_{out_max} * D_{max}] / [f_s * C]$$

Transient time	V_{out} takes longer to settle (time constant = RC)
Ripple	$V_{out} / R_L = I_{out_max}$, so increasing R should reduce the ripple

PRACTICAL DESIGN

PRE-DEFINED PARAMETERS

Parameter	Value
Vin	5V
Vout	12V
Io(max)	0.5A
fs	100kHz
ΔI_L	30%
ΔV_{out}	1%
n	0.9

CALCULATIONS

Parameter	Calculation	Value
RL	$V_{out} / I_{out(max)} = 12 / 0.5$	24Ω
D	$1 - V_{in} / V_{out} = 1 - 5 * 0.9 / 12$	0.625
T	$1 / f = 1 / 100k$	10us
Ton	$D / f = 0.625 / 100k$	6.25us
Pout	$V_{out} * I_{out(max)} = 12 * 0.5$	6W
Pin	$P_{out} / \eta = 6 / 0.9$	6.67W
Iin = IL	$P_{in} / V_{in} = 6.67 / 5$	1.34A
ΔIL	$0.3 * I_L = 0.3 * 1.33$	0.4A
ΔVout	$0.01 * V_{out} = 0.01 * 12$	0.12V
IL(peak)	$I_L + \Delta I_L / 2 = 1.34 + 0.4 / 2$	1.54A
Lmin	$[V_{in} * D] / [f_s * \Delta I_L] = [5 * 0.625] / [100k * 0.4] =$	78.125uH
Cout(min)	$[I_{out(max)} * D] / [f_s * \Delta V_{out}] = [0.5 * 0.625] / [100k * 0.12]$	26.04uF

INDUCTOR, CAPACITOR & DIODE SELECTION


Value	Criterion	Value
L	Close to $L_{min} = 78.125\mu H$	82 μH
I_{pk}	$>I_L(peak) \Rightarrow >1.52 A$	2.1
R_s	Minimum (reduce losses)	0.1204

Value	Criterion	Value
C_{out}	Closest to $C_{out}(min) = 26.04\mu F$	33 μF
V (voltage rating)	$2*V_{out}(max) = 2*12 = 24V$	25V
R_s	Minimum (for lower ripple)	0.06 Ω


Value	Criterion	Value
Type	Schottky diodes for faster switching and low forward voltage drop	82 μH
V_{brkdn}	$>1.5*V_{out} = 18V$	2.1
I_{ave}	$>I_o(max) = 0.5A$	0.1204

MOSFET SELECTION

Value	Criterion	Value
Vds	$2 \cdot V_{out} = 2 \cdot 12 = 24V$	25V
Rds(on)	Minimum (less heat generated)	0.0024
Qg	Minimum (less switching losses)	1.1e-8

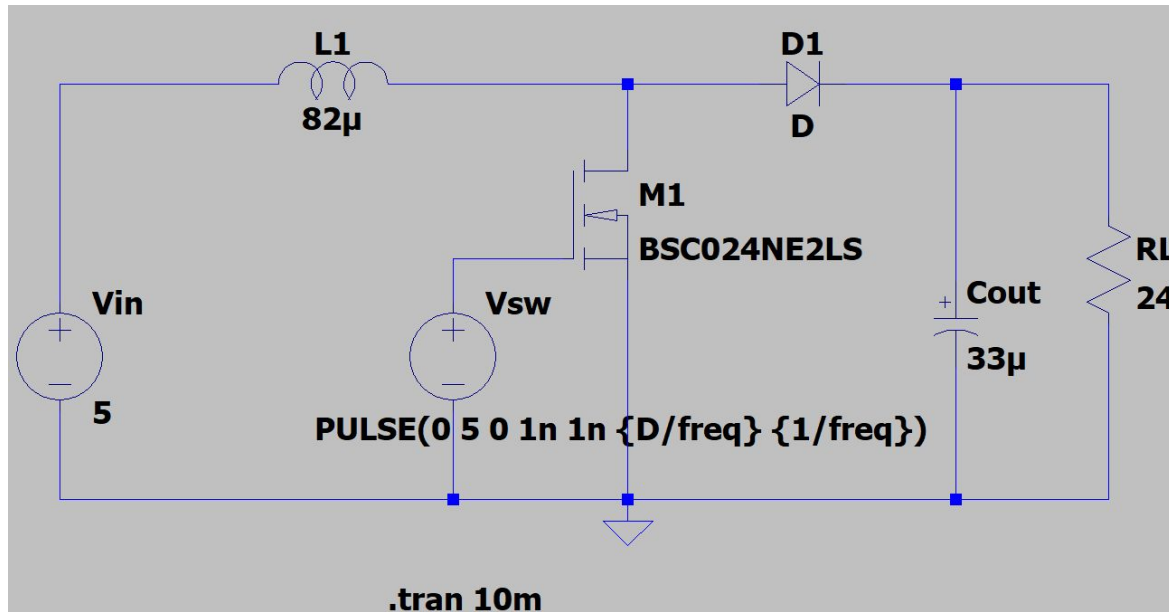


WAVEFORMS

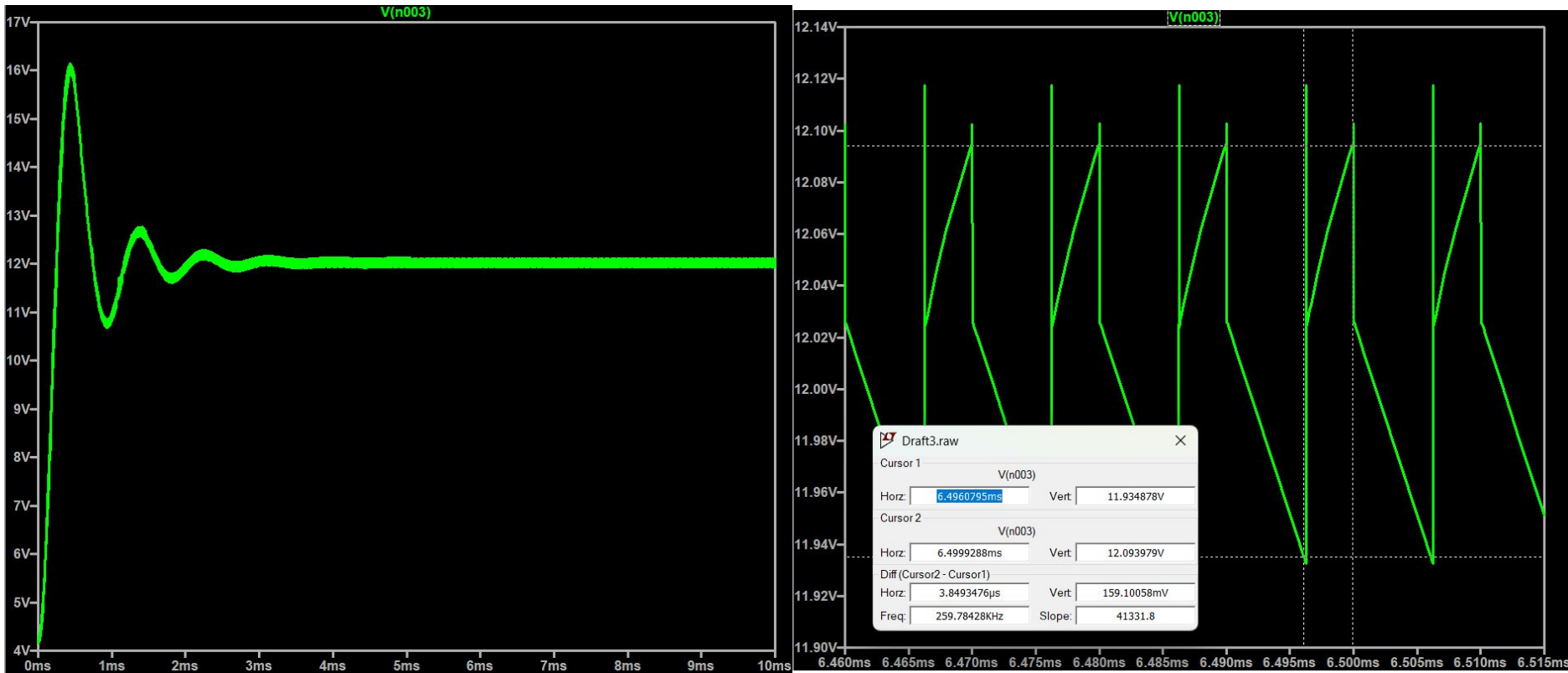

$$\Delta V_{out} = 0.16V$$

WAVEFORMS

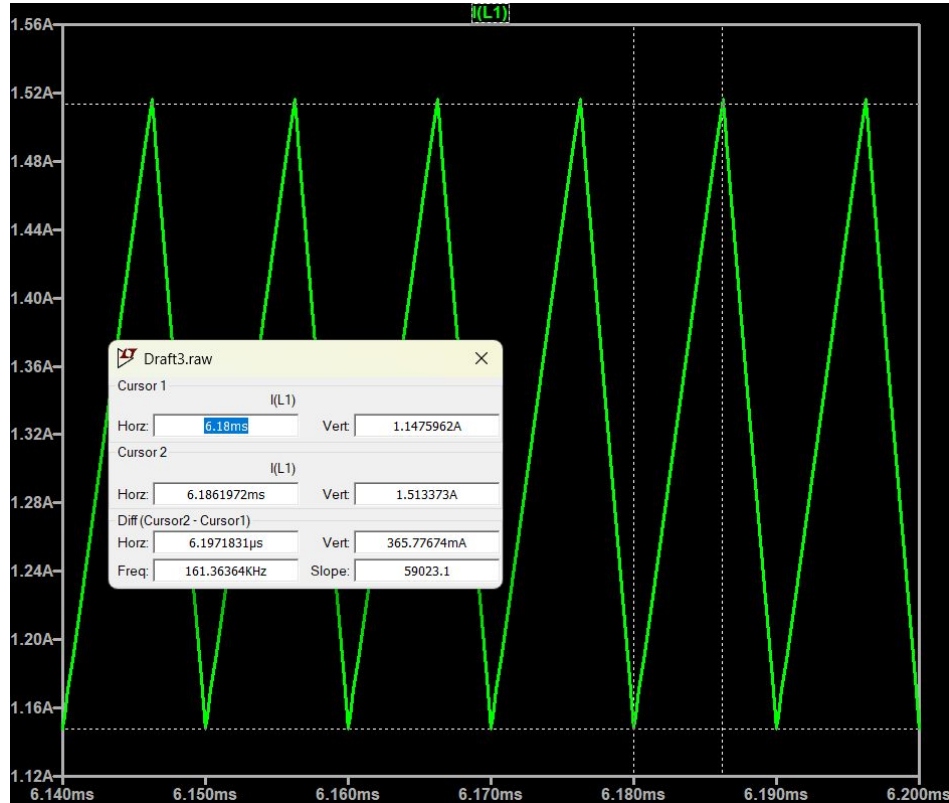

$$\Delta I_L = 0.366A$$

Additional directives

```
.param D=0.625 freq=100k
```

```
.meas Iin avg I(L1) FROM 9m TO 10m
```

```
.meas Vout avg V(n003) FROM 9m TO 10m
```

```
.meas Pin avg -V(n001)*I(Vin) FROM 9m TO 10m
```

```
.meas Pout avg V(n003)*I(RL) FROM 9m TO 10m
```

```
.meas n param Pout*100/Pin
```

RESULTS

Parameter	Expected	Simulated	Absolute Error(%)
lin	1.34	1.332322	0.57
Vout	12	12.010380	0.0865
ΔV_{out}	0.12	0.16	33.33%
ΔI_L	0.4	0.366	8.5%
n	0.9	0.902256	0.25