

## BUCK CONVERTER DESIGN #1

$$D = \frac{V_{out}}{V_{in}} \quad L = \frac{(V_{IN} - V_{OUT}) \cdot D}{f_S \cdot \Delta I_L} \quad I_{L(\text{peak})} = I_{OUT(\text{max})} + \frac{\Delta I_L}{2}$$

$$C_{OUT} = \frac{\Delta I_L}{8 \cdot f_S \cdot \Delta V_{OUT}}$$

Parameter	Value
Input Voltage (Vin)	12 V
Output Voltage (Vout)	5 V
Maximum Output Current (Iomax)	1 A
Switching Frequency (Fs)	500 kHz
Output Voltage Ripple ( $\Delta V_{out}$ )	50 mV
Inductor Current Ripple ( $\Delta I_L$ )	30% of Iomax ~ 0.3 A

Parameter	Calculations	Value
T	1/0.5M	2 us
D	5 / 12	0.417
Ton	0.417 * 2u	0.834 us
L	(12-5) * 0.417 / (0.5Meg*0.3)	19.44 uH
IL(peak)	1 + 0.3 / 2	1.15 A
Cout	0.3 / (8*0.5Meg*50m)	1.5 uF
RL	Vout/ Iomax = 5 / 1	5 A

## INDUCTOR SELECTION

Criterion	Value / Range
Value	Closest to calculated value ~20 uH
Peak current	20-30% more than $I_L(\text{peak}) \Rightarrow 1.3 * 1.15, >1.5A$
Series Resistance	Low as possible to reduce conduction loss.
Material / Frequency	High-frequency power inductor is essential to minimize core loss.

## CAPACITOR SELECTION

Criterion	Value / Range
Equivalent resistance ( $R_{ser}$ )	$\Delta V_{out} = \Delta I_L * R_{ser} \Rightarrow R_{ser} < \Delta V_{out} / \Delta I_L = 50m/0.3, <167m\Omega$ .
Temperature / Voltage Stability	Ceramic capacitors lose capacitance when a DC bias voltage is applied and when the temperature changes. <b>X7R</b> is the <b>standard recommendation</b> for decoupling and filtering in power supplies.
Voltage rating	$>2 * V_{out} = >2 * 5 = >10 V$
Equivalent series inductance	ESL causes high-frequency ringing and is minimized by using small case sizes (e.g., 0805 or 0603) and good PCB layout.

## DIODE SELECTION

Parameter	Formula / Typical Range	Value
Type		Schottky Diode
Breakdown Voltage ( $V_{bkdn}$ )	$1.2 \times V_{in(max)}$	14.4 V
Average Current ( $I_{ave}$ )	$1.2 \times (1 - D) \times I_{out}$	0.7 A
Saturation current ( $I_s$ )	$10^{-9}$ to $10^{-6}$ A	High
Emission Coefficient (N)	1.0 to 1.7	Low close to 1
Series Resistance ( $R_s$ )	10 m $\Omega$ to 100 m $\Omega$	Low

Zero-Bias Junction Capacitance (CJO)	10 pF to 100 pF	Low (otherwise it leads to ringing)
--------------------------------------	-----------------	-------------------------------------


General Schottky Barrier Diodes (SBDs) used:

Series / Part Example	Package Types	Key Feature / Application
1N58xx	DO-41 (Axial), SMA/SMB (SMD)	Industry Standard, Low Cost. Excellent choice for low-power bucks
MBR/MBRS Series	DO-201, SMA/SMB/SMC (SMD)	Very Common SMD parts (e.g., MBRS140, MBRS360).
PDS/SD Series	TO-220, PowerDI, DPAK	Used for <b>medium-power</b> buck converters and general rectification.
SS/B58xx Series	SMC/SMB/SMA (SMD)	High-volume equivalents to MBR parts, often with slightly improved performance.


## MOSFET SELECTION

Parameter	Value	Reason
Drain source voltage (Vds)	$V_{ds} > 1.2 * V_{in(max)} = 14.4 \text{ V}$	The MOSFET must block the full input voltage.
Max Current (Id)	$I_d > 1.5 * I_L(peak) \sim 1.7 \text{ A}$	The MOSFET handles the full inductor current.
Gate-Source Voltage (Vgs)	Vgs (<2V)	
Type	N-channel	N-channel FETs have lower resistance and are standard for the low-side switch
On resistance Rds(on)	Lowest possible ( < 50 mΩ)	Dominant factor for efficiency.
Gate source capacitance (Cgs)	Low	
Gate drain miller capacitance (Cgd)	Low	


## SIMULATION CIRCUIT

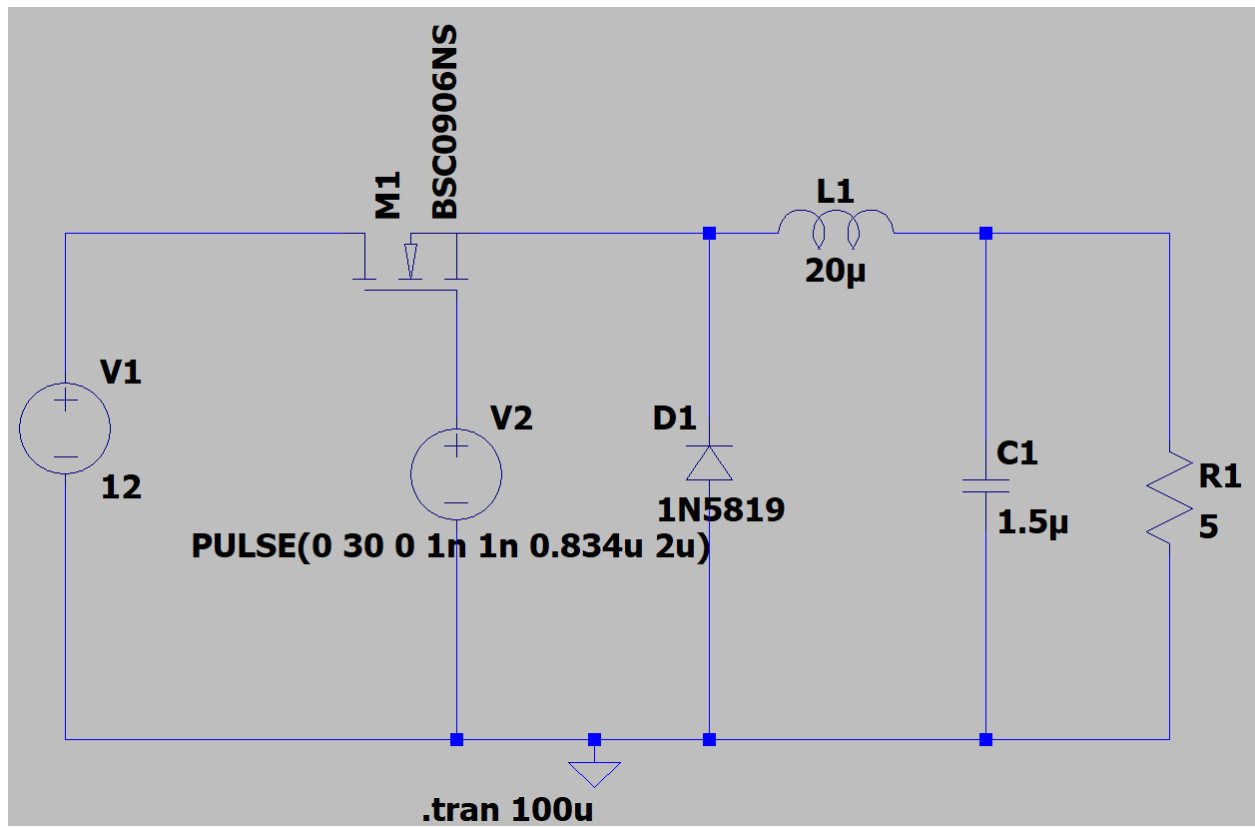


## PLOTS

 

## RIPPLE VOLTAGE

 


## EFFICIENCY CALCULATION

 

Quantity	Calculation	Value
lin(avg)	Observed (-ve sign due to LTSPICE convention for current leaving positive terminal)	-416.85 mA
Pin(avg)	$V_{in}(avg) \cdot I_{in}(avg) = 12 \cdot 416.85m$	5.0022 W
Vout(avg)	Observed	4.6073V
Pout(avg)	$V_{out}(avg)^2 / R_L = 4.6073^2 / 5$	4.245 W
Efficiency	$P_{out}(avg) / P_{in}(avg) \cdot 100 = 4.245 / 5.0022 \cdot 100$	<b>84.87%</b>

## ANALYZING COMPONENT LOSSES

 

Similarly, average power losses are computed for other components.

Quantity	Calculation	Value
Pin(avg)	Observed	5.0022 W
Pout(avg)	Observed	4.4709 W
P(mosfet)	Observed	324.6 mW
P(diode)	Observed	243 mW
P(inductor)	Observed	94.82 mW
P(capacitor)	Observed	171.21 mW
P(gate driver source)	Observed	-298.48mW (supplying power)
Pout (calculated)	Pin - P(Mosfet) - P(Diode) - P(inductor) - P(gate)	4.0413 W
Simulation Gap	Pout(waveform) - Pout(calculated)	0.4296 W

**Rule:** When calculating steady-state efficiency, you should **exclude the capacitor's average power** (or model its loss through ESR) only, which is typically tiny).

Since the P(gate driver source) is so high we vary V(pulse) and obtain following results

V(pulse)	P(pulse)	V(out)	Efficiency
10	-7.9918m	2.8796	33.17
15	-23.106m	4.5834	84.03
20	-301.82m	4.6073	84.91


So V(pulse) of 15 V is selected.

### FINAL MODIFICATIONS TO DUTY CYCLE TO HIT TARGET VOLTAGE

$$D_{new} = D_{current} \times \frac{V_{out, target}}{V_{out, current}}$$

Quantity	Calculation	Value
D(new)	$0.417 * 5 / 4.5834$	0.4549
Ton	$D * T = 0.459 * 2\mu$	9.1 us

### FINAL RESULTS

 

Result: Vout (average) = 5.0533V.